

1. Find V_o and the power supplied by 8 V voltage source in the circuit of Fig.q1.

- 1) Using Nodal Analysis
- 2) Using Mesh Analysis

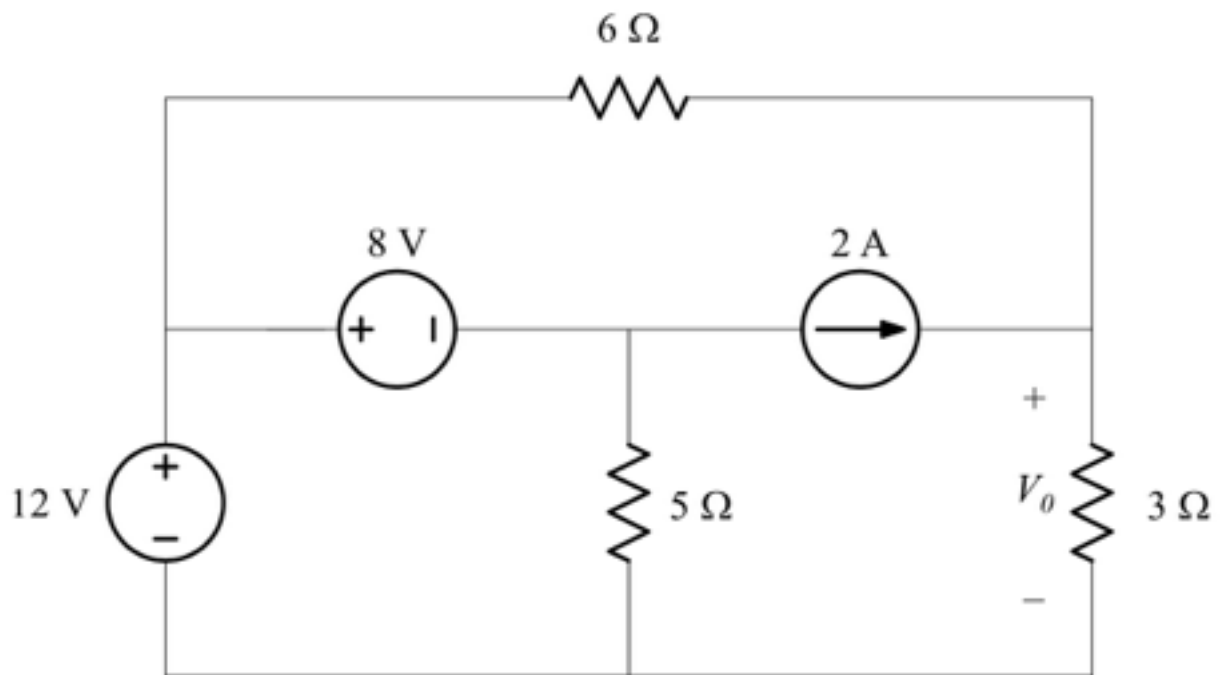


Figure. q1